

# DIGITAL LOGIC

## EXAMPLE PROBLEMS

A	B	C	O
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$O = f(A, B, C)$$

How do I express this truth table?

$$A'B'C + A'BC' + AB'C' + AB'C + ABC' + ABC = O$$

This is the sum of products

A	B	C	O
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$O = f(A, B, C)$$

An alternative way is to express the product of sums.

For the rows where the output is zero, we take the sum of the inverse of the inputs.

$$(A+B+C)*(A+B'+C') = O$$

The two are equivalent:

$$A'B'C + A'BC' + AB'C' + AB'C + ABC' + ABC = (A+B+C)*(A+B'+C') = O$$

# Just for fun

The two are equivalent:

$$A'B'C + A'BC' + AB'C' + AB'C + ABC' + ABC = (A+B+C)*(A+B'+C') = 0$$


$$A'B'C + A'BC' + AB'C' + AB'C + ABC' + ABC = (A'+A)(B'C+BC') + A(BC+B'C'+B'C+BC') = B'C + BC' + A$$

$$\begin{aligned}(A+B+C)*(A+B'+C') &= A+AB'+AC' + AB+BC' + AC+B'C \\ &= A+A(B'+B)+A(C'+C) + BC' + B'C = A + B'C + BC'\end{aligned}$$



## Multiplexer circuit

 1. *Selects* one data channel (from many input channels)
2. *Maps* the selected channel to the output channel



### Sum-of-Products circuit

$D_1 \dots D_4$	:	Data channels
$A, B$	:	Control lines
$F$	:	Output channel

If we want a multiplexer that chooses one of eight possible outputs, how many control signal bits do we need?

If we want a multiplexer that chooses one of three possible outputs, how many control signal bits do we need?

## Decoder circuit

1. **Given**  $n$  control lines
2. **Select** one of  $2^n$  outputs to activate

### Simple AND-gate circuit

$D_1 \dots D_8$  : Output channels

$A, B, C$  : Control lines


*Note:*  $n$  control lines,  $2^n$  outputs

### Laws of Boolean Logic

Regulate circuit function Identity

Law  $1 \wedge A = A, A \in \{0,1\}$

 **Example:** Select  $D_2$ :  $A, C=0$ ;  $B=1$



How many control signal bits are needed to choose one of 32 possible outputs

What should the control signal bits be to choose output 30



# Majority Function

- ➡ Returns 1 if a majority of inputs are high (=1)
- ➡ Formula:  $M(A,B,C) = A'BC + AB'C + ABC' + ABC$


## Truth Table

A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

⇒ **SOP Circuit:**


[Note:  $\bar{A} = \text{NOT}(A)$ ]

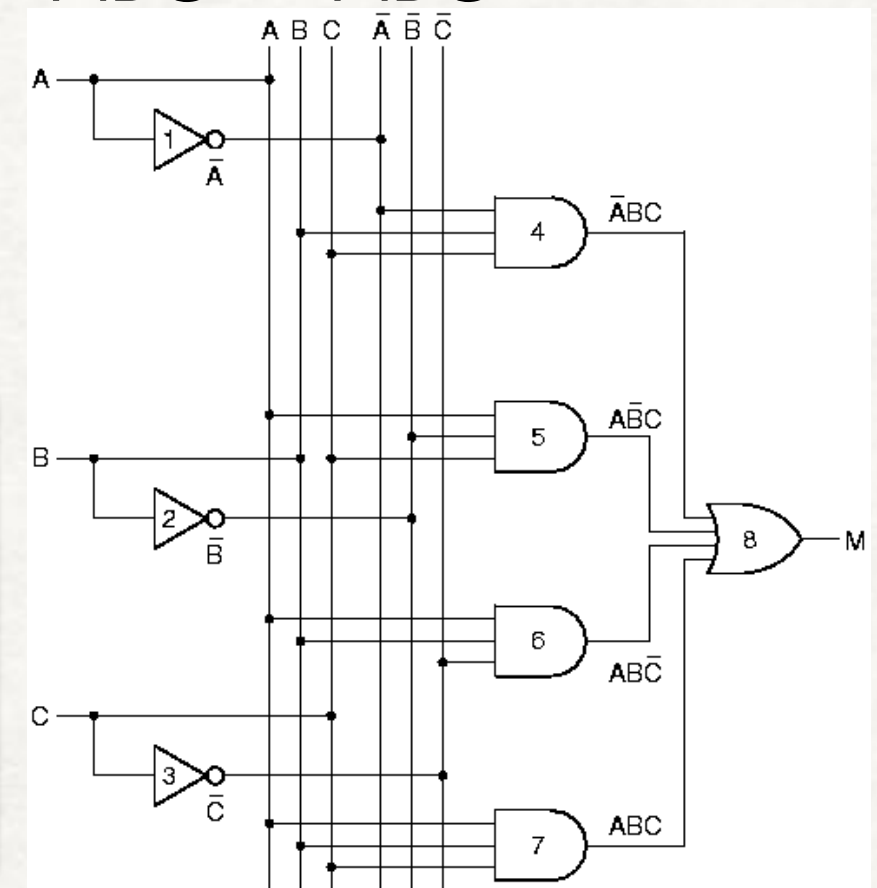Application: In the Space Shuttle, 3 redundant circuits each compute the same function  $f$ . If a MAJORITY of circuit outputs agree (=1), then the 1-valued result is assumed to be correct.




## Comparator circuit

 1. **Given** two  $n$ -bit vectors **A** and **B**
2. **Output** 1 if **A = B**, or 0 otherwise




A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

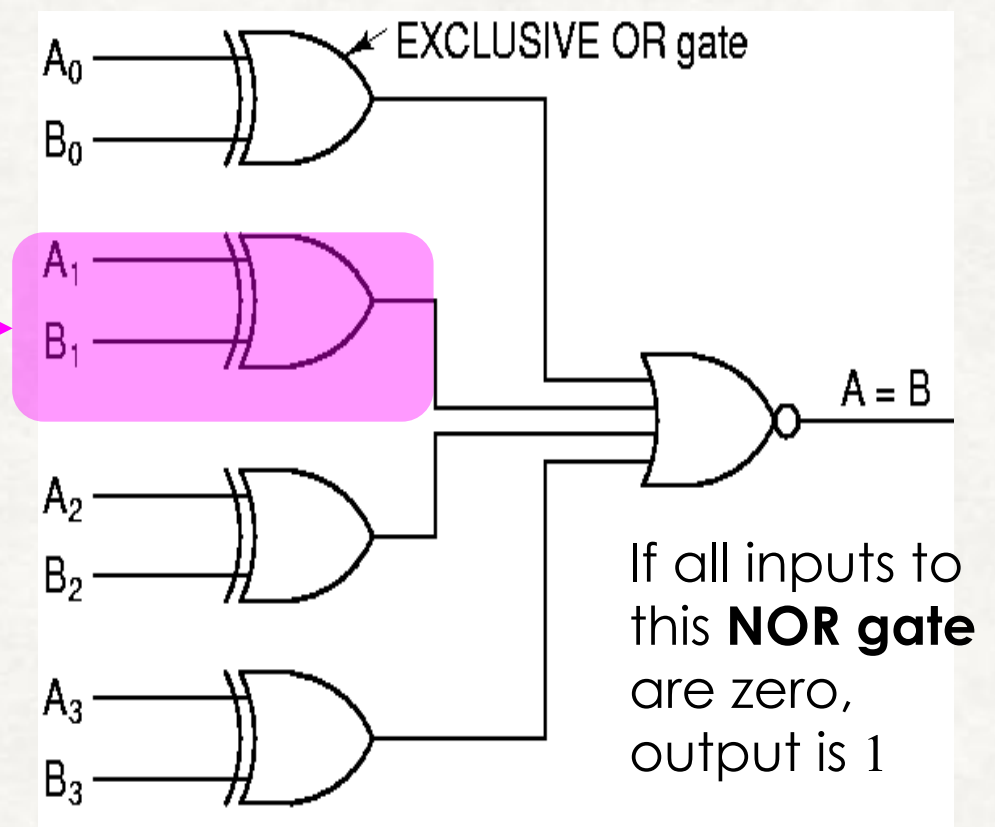

### Laws of Boolean Logic

**Example:** Comparator for Bit  $i$   
outputs 0 if  $A_i = B_i$

# NOR S-R Latch

 


What is this used for?

Memory cell.

How does it work

 The output becomes one when S is asserted. It remains at 1 after S is de-asserted and until R is asserted



An S-R latch begins in the state on the left, with  $Q = 0$  and  $Q' = 1$

What is the value of  $Q$  when  $S$  is set to 1

What is the value of  $Q$  when  $S$  is subsequently set to 0

What is the value of  $Q$  when  $R$  is subsequently set to 1

What is the value of  $Q$  when  $R$  is subsequently set to 0